




- Answer all the following questions
- The exam is in Three Pages

- No. of questions : 5
- Total Mark: 40 Marks

Question (1)

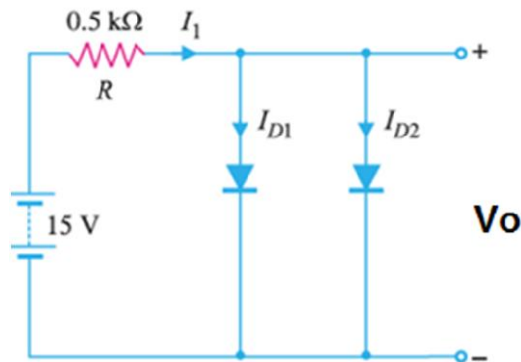
- (a) For the circuit shown below Determine V_o , I_1 , I_{D1} and I_{D2} . Use practical model. Assume diodes to be similar **(5 marks)**



- (b) Draw (only) two different circuits used to clip sine wave signal in positive and negative levels to be like a square wave **(5 marks)**

Question (2)

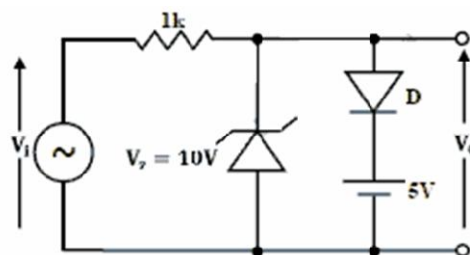- (a) A zener diode used as a regulator at **6.8V**, connected in shunt regulation with unknown load resistance. If the DC input was **5V** and the series resistance between the supply and zener is **10 Ω**, calculate the value of the load resistance that makes the power dissipated through the series resistance be **1W**. **(5 marks)**
- (b) Draw the expected output from the following circuit if the input is with **30V** peak to peak. Assume diode is silicon. **(5 marks)**



1- a

$V_o = 0.7 V$



Solution. The applied voltage forward biases each diode so that they conduct current in the same direction.

$$I_1 = \frac{\text{Voltage across } R}{R} = \frac{15 - 0.7}{0.5 \text{ k}\Omega} = 28.6 \text{ mA}$$

Since the diodes are similar

$$I_{D1} = I_{D2} = \frac{I_1}{2} = \frac{28.6}{2} = 14.3 \text{ mA}$$

1-b

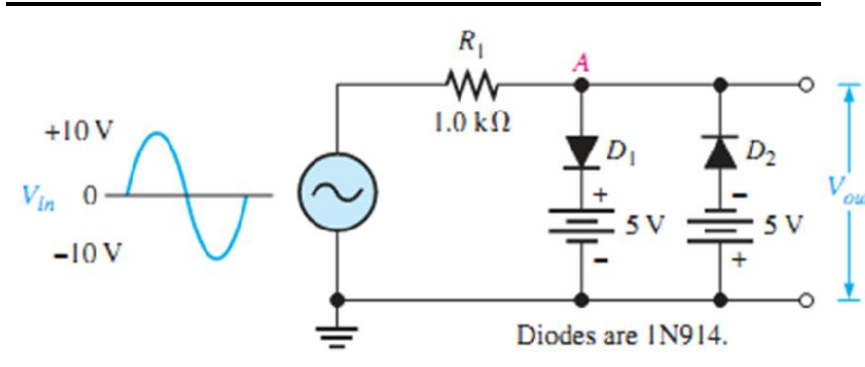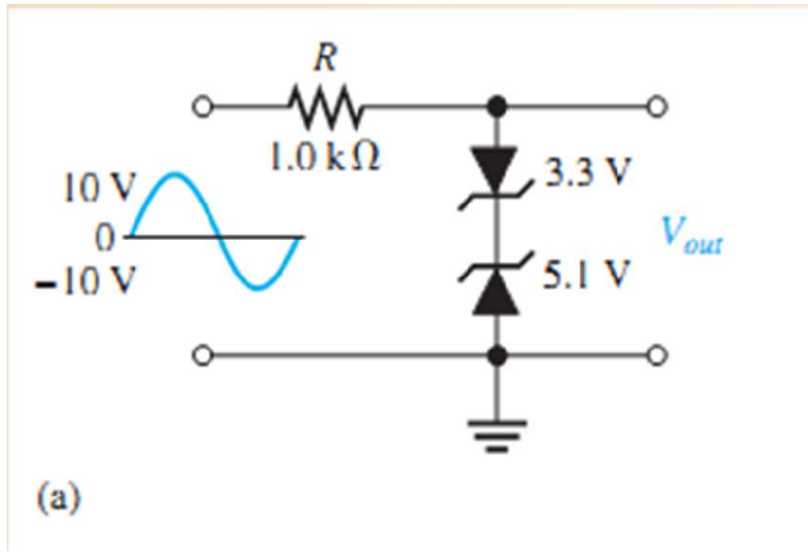

2-a

$$I_s = P / (R_s)^2 = 0.316 \text{ A}$$

$$V_{IN} < V_Z$$

So zener is off (open circuit)

$$\text{So } I_s = I_L = 0.316 \text{ A}$$

$$R_L + R_L = V_{IN} / (I_s) = 5 / 0.316 = 15.8$$

$$R_L = 500 - 10 = 5.8 \ \Omega$$

2-b

