



- Answer all the following questions
- No. of questions: 6
- Illustrate your answers with sketches when necessary.
- Total Mark: 40 Marks

PART II

Q4)

It is required to broadcast a shoubra radio station which detected through FM radio. Design a suitable practical parallel resonance circuit using coil has impedance of $10+j3000\Omega$ to verify the required broadcasting. The circuit has to be heard between (89MHz and 91 MHz) and very clear at 90MHz. (7 marks)

Model answer Final 10Marks

$Z = R_{real} + jX_L = 10 + j3000$
 $f_0 = 90\text{MHz}$
 $BW = 2\text{MHz} \rightarrow f_1 = 89\text{M}$
 $f_2 = 91\text{M}$

Design practical parallel

Convert to ideal

$$R_p = \frac{R^2 + X_L^2}{R} = \frac{10^2 + 3000^2}{10} \approx 900\text{K}$$

$$X_{LP} = \frac{R^2 + X_L^2}{X_L} = \frac{10^2 + 3000^2}{3000} \approx 3000$$

$Q = \frac{f_0}{BW} = \frac{90}{2} = 45$
 $\omega_p = 2\pi f_p = 2\pi \times 90\text{M} = 565.4\text{krad/s}$
 $Q = \frac{X_{LP}}{R_p} = 45 \Rightarrow R_p = \frac{3000 \times 45}{45} = 135\text{K}$
 $\frac{1}{R_{total}} = \frac{1}{900\text{K}} + \frac{1}{R_1} \Rightarrow R_1 = 158.82\text{K}$
 $BW = \frac{1}{RC} = 2 \times 10^6 \times \pi \Rightarrow C = 0.25\text{Pf}$



- Answer all the following questions
- Illustrate your answers with sketches when necessary.
- No. of questions: 6
- Total Mark: 40 Marks

Q5)

Given the following transfer function, $H(s) = \frac{160}{200+2j\omega}$, find the following

requirements: **(6 marks)**

- the type of filter is it?
- the cut off frequency?
- the bandwidth?

In-class Activity 1:
Given the following transfer function, $H(j\omega) = \frac{160}{200+2j\omega}$

a) What type of filter is it?
b) What is the cutoff frequency? 100 rad/s
c) What is the maximum gain? 0.8
d) What is the bandwidth? 100 rad/s

$H(s) = \frac{160}{200+2s} = \frac{80}{s+100} = \frac{K\omega_c}{s+\omega_c}$
 $\omega_c = 100 \text{ rad/s}$

$|H(j0)| \rightarrow \frac{160}{200} = 0.8$
 $|H(j\infty)| \rightarrow 0$

Low-pass Filter

Q6)

For the circuit shown below in figure (1), if $R_L = 2\Omega$; $L = 10\text{mH}$, calculate:

- Obtain the transfer function of the circuit ,
- Justify the type of filter
- Determine the value of C in order to get the minimum value of the modulus of the frequency response for $\omega = 100 \text{ rad/s}$.



- Answer all the following questions
- Illustrate your answers with sketches when necessary.
- No. of questions: 6
- Total Mark: 40 Marks

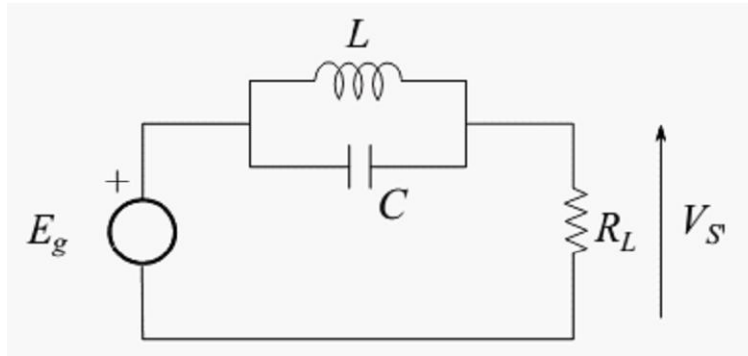


Figure (1)
(7 marks)

3) $C \rightarrow$ min |Freq. response| at $\omega = 100 \text{ rad/s}$

4) 3 dB cutoff freq.

Sol

$$\frac{V_o}{V_{in}} = \frac{R}{R + X_L // X_C} = \frac{1}{1 + \frac{X_L // X_C}{R}}$$
$$= \frac{1}{1 + \frac{(\frac{1}{j\omega C}) \times j\omega L}{j\omega L + \frac{1}{j\omega C}}}$$
$$\frac{V_o}{V_{in}} = \frac{1}{1 + \frac{L/RC}{j(\omega L - \frac{1}{\omega C})}}$$
$$T.F = \frac{1}{1 - j \left(\frac{L/RC}{\omega L - \frac{1}{\omega C}} \right)}$$

$\omega = 0 \rightarrow T.F = 1$
 $\omega = \infty \rightarrow T.F = 1$ band stop filter



Benha University
Faculty of Engineering- Shoubra
Communications and Computer Engineering Program
Final Exam – Term 192 of Academic Year 2018 - 2019
Course: Electric Circuits (2) Code: CCE205
Duration: 2 hours



- Answer all the following questions
- Illustrate your answers with sketches when necessary.
- No. of questions: 6
- Total Mark: 40 Marks

$$TFR = \frac{1}{1 - j \left(\frac{L/Rc}{\omega L - \frac{1}{\omega c}} \right)}$$
$$|TFR| = \frac{1}{\sqrt{1 + \left(\frac{L/Rc}{\omega L - \frac{1}{\omega c}} \right)^2}} \begin{matrix} \rightarrow 0 \\ \rightarrow \infty \end{matrix}$$
$$1 + \frac{L/Rc}{\left(\omega L - \frac{1}{\omega c} \right)^2} = \infty$$
$$\infty = \frac{L/Rc}{\left(\omega L - \frac{1}{\omega c} \right)^2} \rightarrow 0$$
$$\left(\omega L - \frac{1}{\omega c} \right)^2 = 0$$
$$\omega L = \frac{1}{\omega c}$$
$$\omega = \frac{1}{\sqrt{LC}} \neq$$
$$\omega^2 = \frac{1}{LC}$$
$$C = \frac{1}{\omega^2 L} = 10 \mu F$$

$\omega \rightarrow 10 \text{ mH}$